

FEDERAL UNIVERSITY OF TECHNOLOGY OWERRI
SCHOOL OF ENGINEERING AND ENGINEERING TECHNOLOGY
DEPARTMENT OF ELECTRICAL/ELECTRONIC ENGINEERING
2018/2019 RAIN SEMESTER EXAMINATION
ECE 316: Applied Electronics 24th October 2019

Instruction: Attempt Any Five questions of your choice Unit: 3; Time: 3 hours

FOR OPERATIONAL AMPLIFIERS (All questions carry 20 marks)

- 1a. In a tabular form, compare an ideal operational amplifier (op-amp) and a real op-amp with respect to their input resistance R_i , output resistance R_o and open loop gain A . Give the two primary equations that define an ideal op-amp completely. (5 marks)
- 1b. Draw the equivalent circuit of a real op-amp and its characteristic curve showing the output voltage v_o as a function of the differential input voltage v_d (Indicate all regions). (5 marks)
- 1c. An instrumentation amplifier shown in Fig.1 is an amplifier of low-level signals used in process control or measurement applications and commercially available in single-package units. Given that amplifier A_3 is a difference amplifier, show that (complete derivation) (10 marks)

$$v_o = \frac{R_2}{R_1} \left(1 + \frac{2R_3}{R_4} \right) (v_2 - v_1)$$

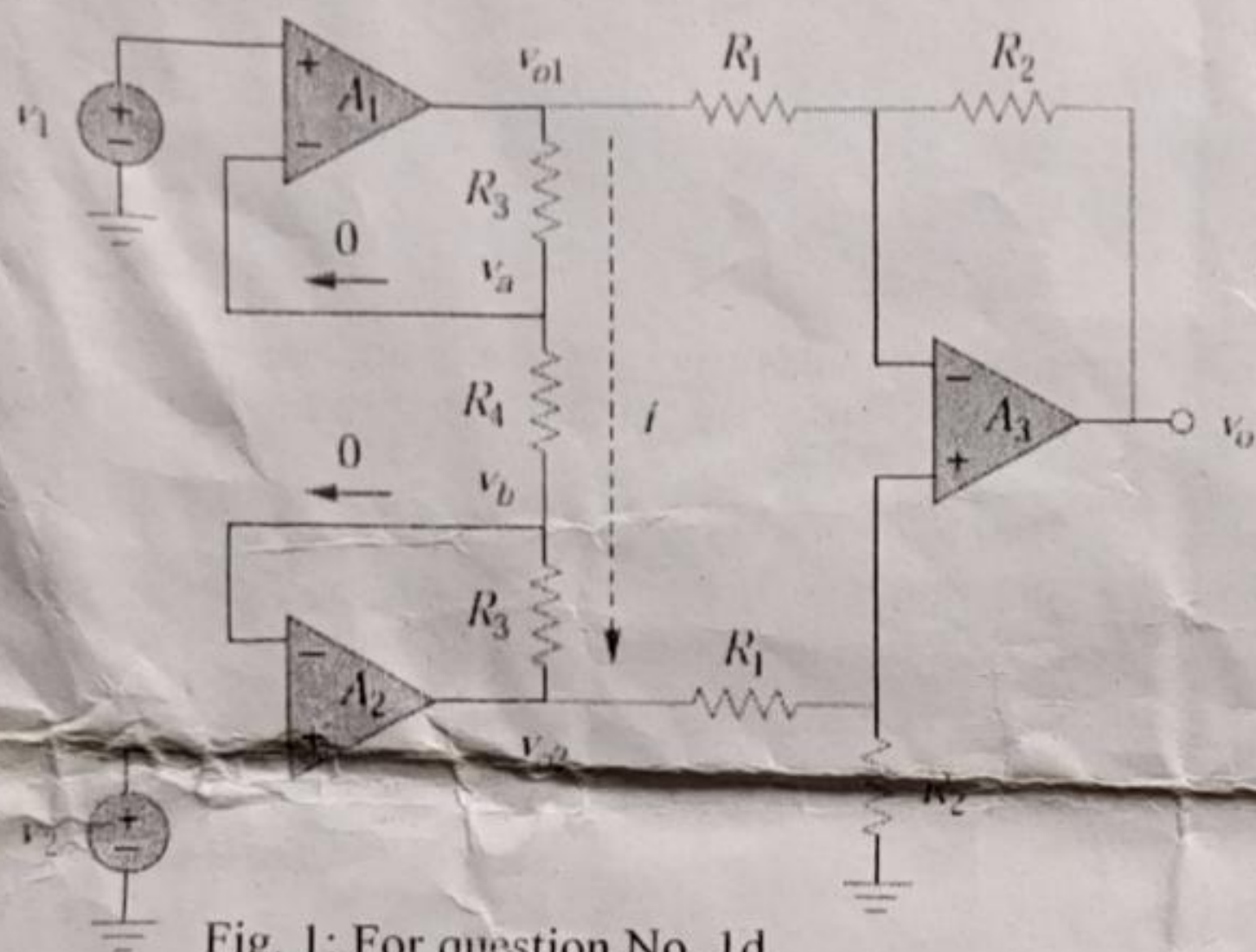


Fig. 1: For question No. 1d

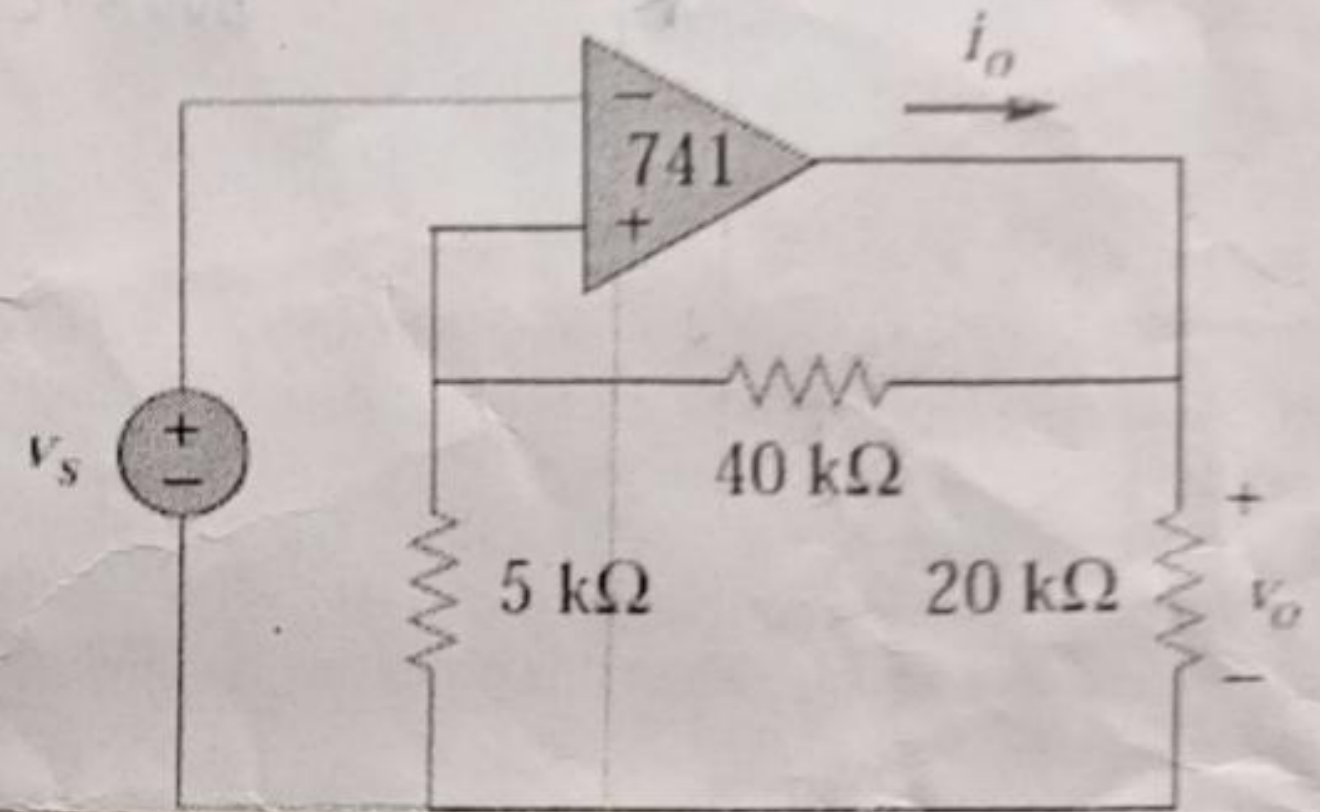


Fig. 2: For question No. 2a

- 2a. A 741 op-amp has an open-loop voltage gain of 2×10^5 , input resistance of $2M\Omega$ and output resistance of 50Ω . The op amp is used in the circuit of Fig2. Find the closed-loop gain v_o/v_s and determine current i_o when $v_s = 1V$. (10 marks)
- 2b. Confirm the two solutions obtained in question 2a by considering the op-amp as an ideal op-amp. (5 marks)
- 2c. List only five applications of an op-amp in electrical, electronic or control circuitries. (5 marks)

FOR BREAKDOWN DEVICES (All questions carry 20 marks)

- 3a. The phase control circuit of Fig. 3 is connected to an ac supply $v = 60 \sin \theta$ and load $R_L = 50\Omega$. Gate current is $100\mu A$ and gate voltage $0.5V$. Determine the range of adjustment of R for the silicon-controlled rectifier (SCR) to be triggered between 30° and 60° . Take the diode barrier voltage to be $0.7V$. (5 marks)
- 3b. List three methods of turning on and two methods of turning off an SCR. (5 marks)
- 3c. List five applications of a silicon-controlled rectifier. (5 marks)
- 3d. The two-transistor analogy of an SCR has the following data: PNP transistor gain = 0.4; NPN transistor gain = 0.5; gate current $I_G = 50mA$. Calculate the anode current I_A of the device. (5 marks)

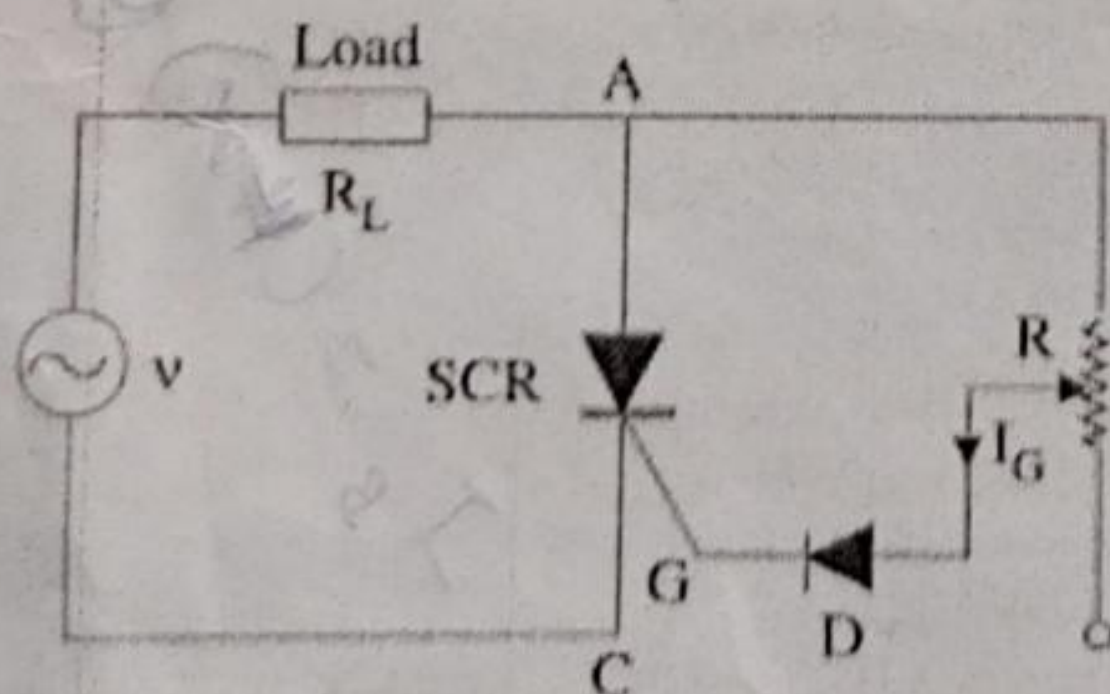


Fig. 3: For question No. 3a

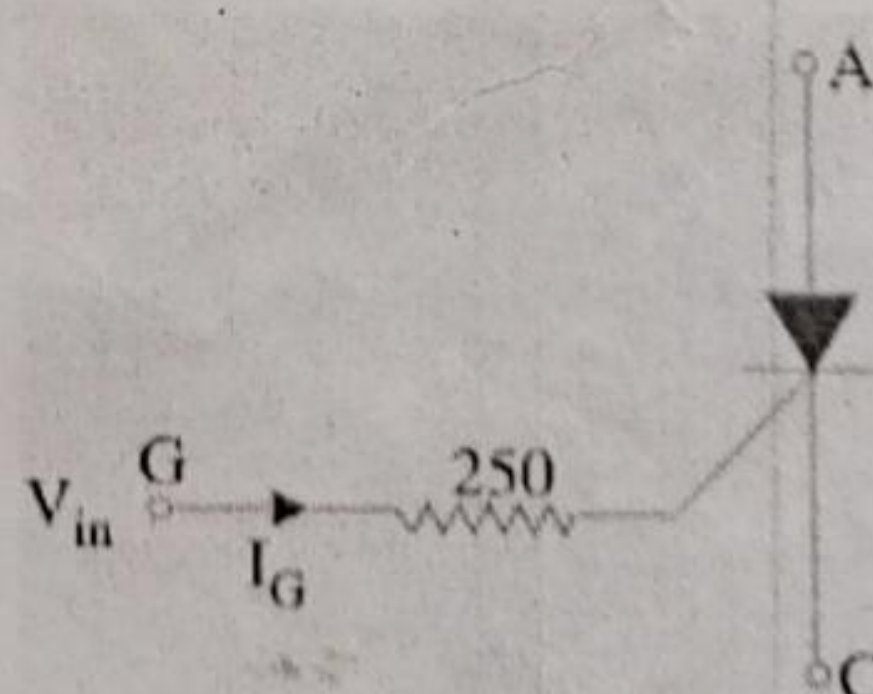


Fig. 4: For question No. 4b

- 4a. Describe the following thyristors using only their detailed electronic symbol, PN structure and IV characteristic.
- i) Silicon controlled rectifier (3 marks)
 - ii) Triode ac (3 marks)
 - iii) Diode ac (3 marks)
 - iv) Unijunction Transistor (3 marks)

$$V = I_{G1}R_1 + I_{G2}R_2 + V_G + V_D$$

4b. A $250\ \Omega$ resistor is connected in series with the gate of an SCR as shown in Fig 4. The gate current required for firing the SCR is 8mA . Calculate the value of the input voltage V_{in} required for causing the SCR to breakdown. (4 marks)

4c. Thyristors are otherwise known as breakdown devices due to a phenomenon called avalanche breakdown. Thus, differentiate between avalanche breakdown and Zener breakdown. (4 marks)

5a. Outline seven major considerations (parameters) while using a Bipolar Junction Transistor (BJT) for electronic circuit design. Explain three of them (6 marks)

5b. In a Transistor configuration, $V_{CC} = +35\text{V}$, biasing resistors connected in voltage-divider pattern with $R_1 = 2550\ \Omega$, $R_e = 900\ \Omega$ and $R_2 = 11450\ \Omega$. Calculate the bias voltage (3 marks)

(c) Sketch the symbol of complementary metal oxide semiconductor <CMOS>, label all the terminals and state 2 applications of this component (4 marks)

(d) A BJT circuit shown in figure 5 has a current gain (β) of 50 and Emitter-Base voltage V_{BE} of 600mV . Determine the Emitter-Collector Voltage V_{EC} in volts (7 marks)

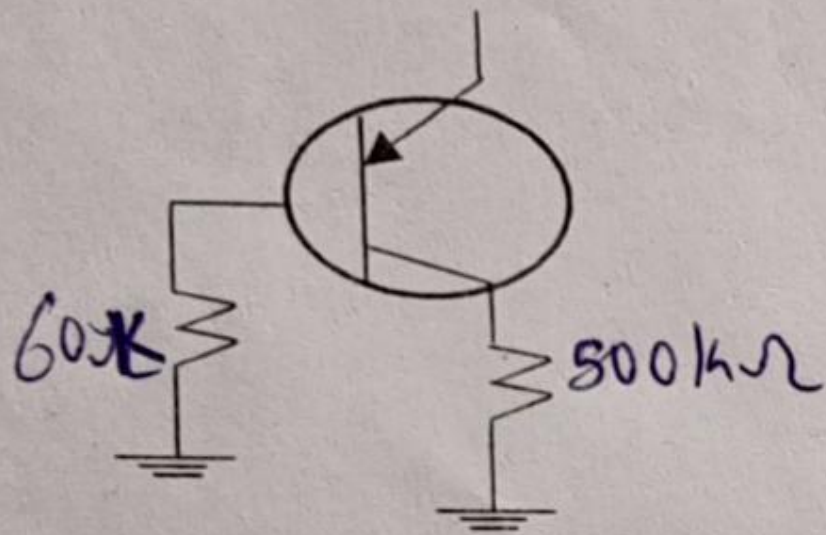


Fig 5: A PNP transistor

6a. With the aid of circuit diagram, explain the 3 types of BJT configuration and their respective main applications (5 marks)

6b. Sketch the input and output characteristics of a common Emitter BJT configuration. From there, determine the Q-point and internal resistance (r) respectively (6 marks)

6c. Compare MOSFET types with JFET types by sketching their symbols only (4 marks)

6d. A common based current gains of a BJT is 0.92 and its collector base junction reverse bias saturation current $I_{CO} = 0.45\ \mu\text{A}$. Determine the collector current I_C , when this transistor is connected in CE mode and operated in the active region with base current I_B of $16\ \mu\text{A}$ (5 marks)