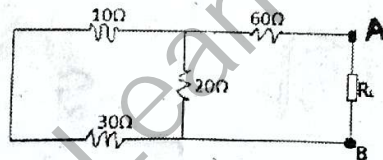


FEDERAL UNIVERSITY OF TECHNOLOGY, OWERRI
SCHOOL OF PHYSICAL SCIENCES
DEPARTMENT OF PHYSICS
2015/2016 HARMATTAN SEMESTER Time: 3hrs
PHY 201: APPLIED ELECTRICITY I Date: 27/04/16

Instruction: Answer Question ONE and any other three questions.

QUESTION 1

- a) A 45Ω resistor is connected to the terminate of a battery whose emf is 12.0v and whose internal resistance is 0.5Ω . Calculate the current in the circuit.
- b) i. Define the resistivity of a copper wire.
ii. A copper wire in a typical house has a diameter of about 1.5mm . How long would a wire be in order to have a resistance of 10.0Ω , if the resistivity is $1.68 \times 10^{-8}\Omega\text{m}$?
- c) A voltage source having emf of 12v and internal resistance of 1Ω is connected to two resistors of 4Ω and 8Ω connected in parallel,
 - i. Draw and label the circuit
 - ii. What is the current flowing through the 8Ω resistor?
- d) An electric current of 10A is divided into three branches of resistors R_1, R_2 and R_3 with resistances of $1\Omega, 2\Omega$ and 3Ω respectively.
 - i. Draw the circuit diagram
 - ii. Find the current in each branch of the circuit.
- e) What is the load resistance R_L that will ensure maximum power transfer in the circuit shown below?




- f) i. What is Peak-to-peak value of an alternating waveform?
ii. A supply voltage has a mean value of 250V .
Calculate (a) the maximum value
(b) The rms value
(c) The peak factor of the supply voltage
- g) In a single phase series a.c. circuit containing only purely capacitance, draw and label the following
 - (a) the circuit diagram
 - (b) the current and voltage waveform
 - (c) the phasor diagram. Comment how the current and voltage relate in the circuit diagram.
- h) A coil having a resistance of 6Ω and an inductance of 0.03H is connected across a $100\text{V}, 50\text{Hz}$ sine wave supply. Calculate (i) the impedance (ii) the power factor
- i) What is a j-operator in an a.c. circuit?

QUESTION 2

- Explain the potential difference between two points in a circuit.
- What is the kilo-watt hour (kw-h)? What is the equivalent in Joules?
- Two coils which are close together have a mutual inductance of 330mH. If the emf in the coil is 120V, what is the rate of change of the current in coil 2?

QUESTION 3

- State the two Kirchoff's laws
- State the superposition theorem.
 - Using superposition theorem only, calculate the voltage drop over R_2 in the circuit shown below.

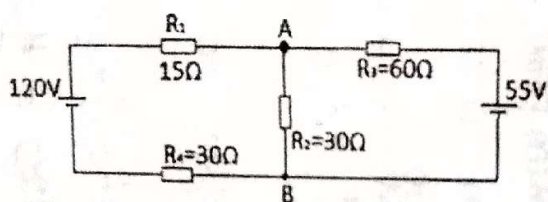

QUESTION 4

- Draw the circuit diagram, the current and voltage waveforms and the phasor diagrams for the following single phase series a.c. circuit.
 - Purely resistive a.c. circuit
 - Purely inductive a.c. circuit
 - Comment on the current and voltage relationships in each
- A current of 5A flows through an a.c. circuit containing a resistor of resistance 8Ω and two reactances $X_L = 6\Omega$ and $X_C = 12\Omega$
 - Obtain the p.d across each element
 - Calculate (1) the impedance and the effective voltage of the circuit (2) the phase angle between voltage and current.

QUESTION 5

- Draw phasor diagram for the following:
 - Series R-L-C and
 - Parallel R-L-C circuits of resonance
- A circuit of $(6 + j8)\Omega$ passes through a resistor of resistance 2Ω in an a.c. circuit. What is the power dissipated on the resistor?
- An a.c. circuit having a resistance of 50Ω and a capacitance of $40\mu\text{F}$ are connected across a 230V, 50Hz supply.
Calculate (i) the current in the circuit (ii) the phase of the current relative to the applied voltage
(iii) express the impedance in rectangular and polar notations.


2015/2016 EXAM SOLUTIONS

a $E = I(r+R); I = \frac{E}{r+R}$
 Given $E = 12V, R = 45\Omega$ and $r = 0.5\Omega$
 $I = \frac{12}{0.5+45} = \frac{12}{45.5} = \underline{\underline{0.26A}}$

b i) The resistivity of a copper wire is the resistance of a unit length of a copper wire with uniform cross-sectional area.

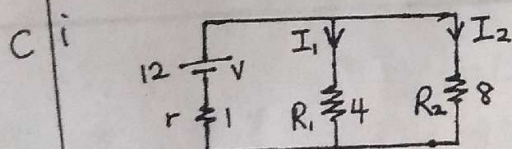
ii) Given $d = 1.5mm = 1.5 \times 10^{-3}m, R = 10\Omega$
 $P = 1.6 \times 10^{-8} \Omega m$
 $P = \frac{RA}{L} \Rightarrow L = \frac{RA}{P}$
 but $A = \frac{\pi d^2}{4} = \frac{\pi (1.5 \times 10^{-3})^2}{4} = 1.76 \times 10^{-6} m^2$

$\therefore L = \frac{10 \times 1.76 \times 10^{-6}}{1.6 \times 10^{-8}} = \underline{\underline{1104.5m}}$



ii) $R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{4 \times 8}{4 + 8} = \frac{32}{12} = 2.67\Omega$


The diagram becomes

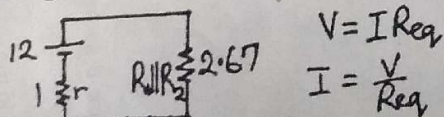

$I = \frac{12}{2.67+1} = 3.27A$

$I_1 = \frac{I R_2}{R_1 + R_2} = \frac{3.27 \times 8}{8 + 4} = \underline{\underline{2.18A}}$

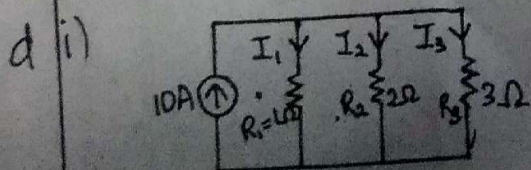$I_2 = \frac{I R_1}{R_1 + R_2} = \frac{3.27 \times 4}{8 + 4} = \underline{\underline{1.09A}}$




ii) $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = 1 + \frac{1}{2} + \frac{1}{3} = \frac{11}{6}$
 $R_{eq} = \frac{6}{11} = 0.54\Omega$

$I_1 = \frac{R_{eq} \cdot I}{R_1} = \frac{0.54 \times 10}{1} = \underline{\underline{5.4A}}$

$I_2 = \frac{R_{eq} \cdot I}{R_2} = \frac{0.54 \times 10}{2} = \underline{\underline{2.7A}}$

$I_3 = \frac{R_{eq} \cdot I}{R_3} = \frac{0.54 \times 10}{3} = \underline{\underline{1.8A}}$

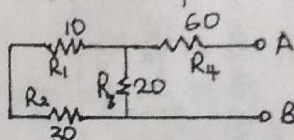e) Maximum power transfer occurs when $R_L = R_{TH}$ so to find R_{TH} , we remove R_L



Due to open circuit, no current flows through R_4 i.e.

$R_{TH} = (R_1 + R_2) || R_3 + R_4 = (30 + 10) || 20 + 0$
 $= 40 || 20 = \frac{40 \times 20}{40 + 20}$

$R_{TH} = 13.33\Omega$

\therefore For MPT to occur, $R_L = 13.33\Omega$

f) i. This is the value between the negative and positive vertical direction of a waveform.



ii) a. The mean value is also called the average value

$V_{av} = 0.637 V_m$


$\therefore V_m = \frac{V_{av}}{0.637} = \frac{250}{0.637} = \underline{\underline{392.46V}}$

b. $V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{392.46}{\sqrt{2}} = \underline{\underline{277.5V}}$

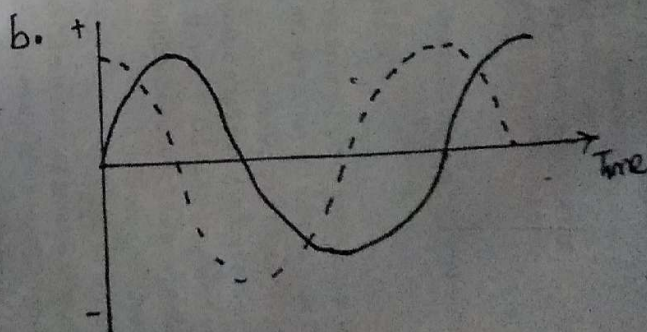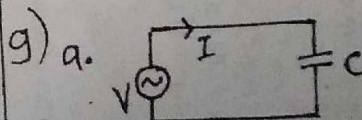c. $K_a = \frac{\text{max value}}{\text{rms value}} = \frac{V_m}{V_{rms}} = \frac{392.46}{277.5} = \underline{\underline{1.41}}$



current = - - - - -
 voltage = _____

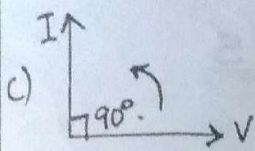

Voltage lags by 90° or
Current leads by 90° in
a purely capacitive circuit

h i. $Z = \sqrt{R^2 + X_L^2}$

Given $R = 6\Omega$, $X_L = \omega L = 2\pi fL = 2\pi \times 50 \times 0.03$
 $X_L = 9.42\Omega$

$Z = \sqrt{6^2 + 9.42^2} = 11.16\Omega$

ii. Power factor = $\frac{R}{Z} = \frac{6}{11.16} = 0.54$

i A j-operator is used to represent a complex part of a parameter in an AC circuit.

QUESTION 2

a The potential difference between two points in a circuit is the energy required to move a positive test charge from one of the points to the other in the circuit. (Also see variant in 2013/14 exam No1)

b Kilowatt hour (kw-h) is a measure of electrical energy equivalent to a power consumption of 1000 watts for 1 hour

$1\text{kw} = 1000\text{Watt} = 1000\text{J/s}$

$1\text{kw-h} = 1000\frac{\text{J}}{\text{s}} \times 3600\text{s} = 3600000\text{J}$

$\therefore 1\text{kwh} = 3.6\text{MJ}$

c $V_i = M_{12} \frac{di_2}{dt}$

given $M_{12} = 330\text{mH} = 330 \times 10^{-3}\text{H}$, $V_i = 120\text{V}$


$\therefore \frac{di_2}{dt} = \frac{V_i}{M_{12}} = \frac{120}{330 \times 10^{-3}} = 363.64\text{A/s}$

QUESTION 3

a Same as 2014/2015 test - 3a

b i) Same as 2014/2015 exam - 1g

ii) When 120V is acting alone,

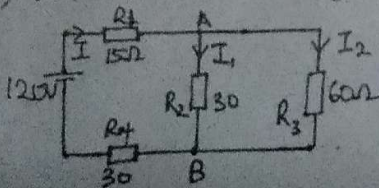

$R_{eq} = R_1 + R_4 + R_2 || R_3 = 15 + 30 + \frac{30 \times 60}{30 + 60}$


$R_{eq} = 65\Omega$

$I = \frac{V}{R_{eq}} = \frac{120}{65} = 1.85\text{A}$

$\therefore I_1 = \frac{I R_3}{R_2 + R_3} = \frac{1.85 \times 60}{60 + 30} = 1.23\text{A}$

$I_2 = \frac{I R_2}{R_2 + R_3} = \frac{1.85 \times 30}{60 + 30} = 0.62\text{A}$

When 55V is acting alone,

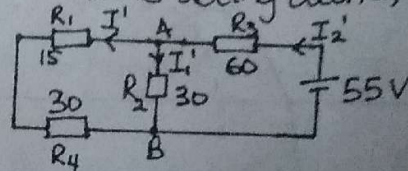

$R_{eq} = (R_1 + R_4) || R_2 + R_3$

$= \frac{(15 + 30)(30)}{(15 + 30) + 30} + 60 = \frac{45 \times 30}{45 + 30} + 60$

$R_{eq} = 18 + 60 = 78\Omega$

$\therefore I_2' = \frac{V}{R_{eq}} = \frac{55}{78} = 0.71\text{A}$

$I_1' = \frac{I_2' \times (R_1 + R_4)}{R_2 + (R_1 + R_4)} = \frac{0.71 \times 45}{45 + 30} = 0.43\text{A}$



$I_1' = \frac{I_2' R_2}{R_2 + (R_1 + R_4)} = \frac{0.71 \times 30}{45 + 30} = 0.28\text{A}$



Superimposing to get current in branch AB,
 $I_1 + I_1' = 1.23 + 0.43 = 1.66\text{A}$

Since the current across $R_2 = 1.66\text{A}$, then voltage drop over R_2 is


$V = IR = 1.66 \times 30 = 49.8\text{V}$

QUESTION 4

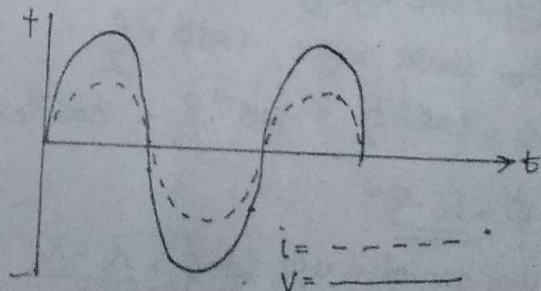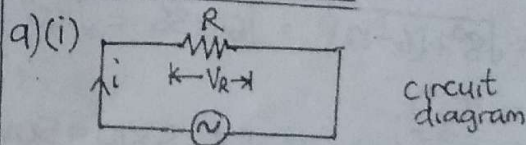

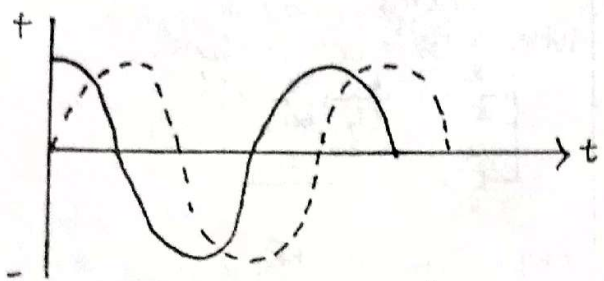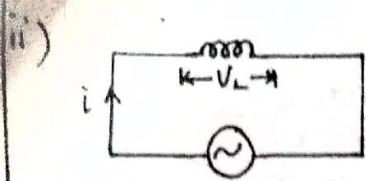

current = - - - - -
voltage = ———

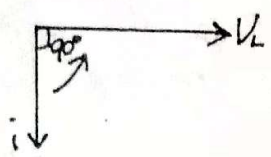

iii) For purely resistive, current and voltage has no phase difference
For purely inductive voltage leads or current lags by 90°

b) i) $V_R = IR = 5 \times 8 = \underline{40V}$
 $V_L = IX_L = 5 \times 6 = \underline{30V}$
 $V_C = IX_C = 5 \times 12 = \underline{60V}$

ii) Impedance $Z = \sqrt{R^2 + (X_L - X_C)^2}$
 $Z = \sqrt{8^2 + (6 - 12)^2} = \sqrt{64 + 36} = \sqrt{100}$
 $Z = \underline{10\Omega}$



Effective voltage $V = IZ = 5 \times 10 = \underline{50V}$

For phase angle, $\cos \phi = \frac{R}{Z}$
 $\phi = \cos^{-1} \frac{R}{Z} = \cos^{-1} \frac{8}{10} = \cos^{-1} 0.8$

$\phi = \underline{36.9^\circ}$

you can also use $\tan \phi = \frac{X_L - X_C}{R}$

QUESTION 5

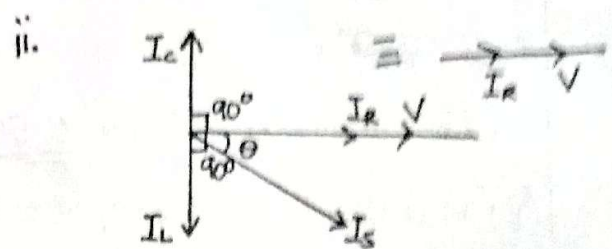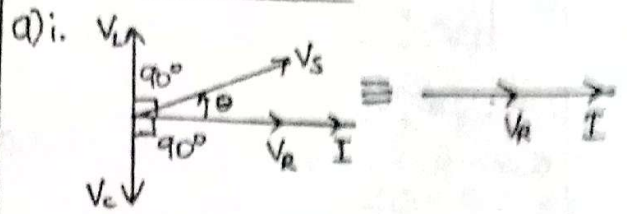

b) $P = I^2 R$
 given $I = 6 + j8$, $R = 2\Omega$
 $P = (6 + j8)^2 \times 2 = (36 + j48 + j48 - 64) \times 2$
 $P = \underline{(-56 + j192)W}$

c) i) $V = IZ$
 but $Z = \sqrt{R^2 + X_C^2} = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} = \sqrt{R^2 + \left(\frac{1}{2\pi f C}\right)^2}$
 given $R = 50\Omega$, $f = 50\text{Hz}$, $C = 40\mu\text{F} = 40 \times 10^{-6}\text{F}$
 $Z = \sqrt{50^2 + \left(\frac{1}{2\pi \times 50 \times 40 \times 10^{-6}}\right)^2} = 93.98\Omega$

$\therefore I = \frac{V}{Z} = \frac{230}{93.98} = \underline{2.45A}$

ii) $\tan \phi = \frac{X_C}{R}$
 $X_C = \frac{1}{2\pi \times 50 \times 40 \times 10^{-6}} = 79.58$

$\phi = \tan^{-1} \frac{X_C}{R} = \tan^{-1} \frac{79.58}{50}$
 $= \tan^{-1} 1.59 = 57.85$

$\phi = -57.85^\circ$

iii) Here impedance $Z = 93.98\Omega$

$\therefore Z = (93.98 + j0)\Omega \rightarrow \text{Rectangular}$

$Z = (93.98 \angle 0^\circ)\Omega \rightarrow \text{Polar}$