



AIR FORCE INSTITUTE OF TECHNOLOGY
FACULTY OF GROUND AND COMMUNICATION ENGINEERING
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
SECOND SEMESTER EXAMINATION 2020/2021
B.sc IN ELECTRICAL & ELECTRONIC ENGINEERING

Course Title: ANALOGUE ELECTRONICS
Course Code: EEE 306
Credit Unit: 2 Units
Instruction: ANSWER ANY FOUR QUESTION OUT OF SIX (6)
Duration: 2 HOURS
Date: 25th January, 2022

Question 1

- a. Give two areas of application of bipolar junction transistors (BJT). (2 marks)
- b. Accompanied with a clear diagrams give a concise description of NPN and PNP transistors. (5 marks)
- c. Define the following part of transistors
- i. Base, (2 marks)
 - ii. Emitter and, (2 marks)
 - iii. Collector. (2 marks)
- d. For proper working of a transistor, what are the golden rules in biasing it? (2 marks)

Question 2

- a. With the aid of a diagram, explain what is a pn junction (3 marks)
- b. With the aid of diagrams differentiate between forward and reverse bias of pn junction (6 marks)
- c. Explain the following terms
- i. Depletion region (2 marks)
 - ii. Potential barrier (2 marks)
 - iii. Built-in potential (2 marks)

Question 3

- a. Draw a diagram showing a common emitter configuration of a bipolar transistor and derive the equations relating α and β . (5 marks)
- b. In a common base configuration, current amplification factor is 0.9. if the emitter current is 1mA, determine the value of base current (5 marks)
- c. In a common base configuration, $\alpha = 0.95$. The voltage drop across a $2k\Omega$ resistor which is connected in the collector is 2V. find the base current. (5 marks)

Question 4

For the following Voltage regulating circuit diagram below in Fig 1, Provide (Draw clearly) the complete circuit to represent



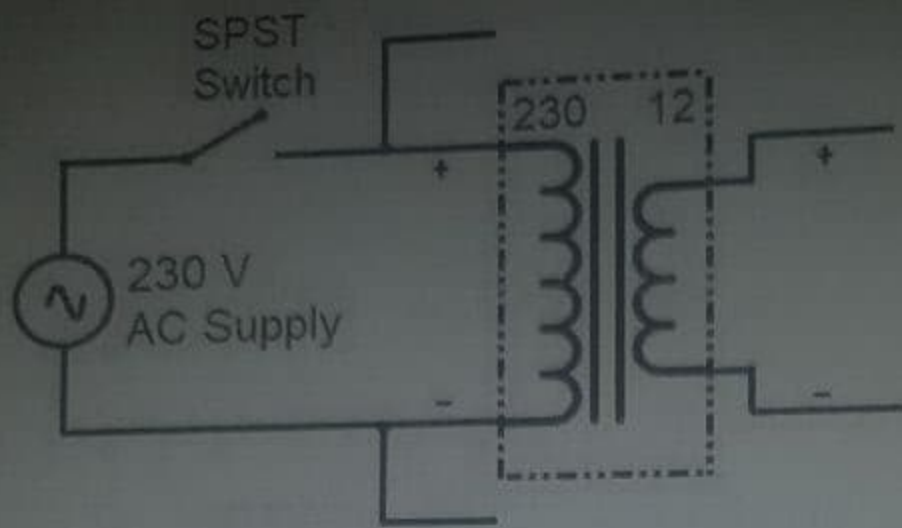


Fig. 1

- Voltage Buck Operation (2 marks)
- Voltage Boost Operation (2 marks)
- Explain Voltage regulation with Buck operation and calculate the value of A for Buck Operation (3 marks)
- Explain Voltage regulation with Boost operation and calculate the value of A for Boost Operation (3 marks)
- Stabilizers are typically high efficiency devices which generally operate in what efficiency range? (1 marks)
- List two consequences of Over Voltage in Electronic Equipment (2 marks)
- List two consequences of Under Voltage in Electronic Equipment (2 marks)

Question 5

- With a well labeled diagram explain what you understand by the term operational amplifier (3 marks)
- Draw clearly the circuit symbol of an operational amplifier showing both the inverting and non-inverting terminals (3 marks)
- State the configuration in which an operational amplifier operates (3 marks)
- With the aid of a well labeled circuit diagram, explain the term Virtual grounding in an operational amplifier (3 marks)
- Explain in details the reason why input voltage (V_i) is reduced to almost zero in an operational amplifier (3 marks)

Question 6

- Find the value of output voltage of an operational amplifier as an inverting adder for the following sets of input voltages and Resistance, in all cases $R_F = 1M\Omega$ (3 marks)
 $V_1 = -3V, V_2 = +3V, V_3 = +2V, R_1 = 250K\Omega, R_2 = 500K\Omega, R_3 = 1M\Omega$



