

FEDERAL UNIVERSITY OF TECHNOLOGY OWERRI
SCHOOL OF ENGINEERING AND ENGINEERING TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
ECE 302 (Theory of Electronic Instrumentation and Measurement) Examination

Instruction: Answer any two questions from Section A and any two questions from Section B. Each question carries 20 marks
 Date: 21/09/16 Session: 2015/2016 Unit: 2 Time Allowed: 3 Hours

SECTION A: Answer any two questions from this section

1. (a) Define measurement. (b) Draw a neat circuit diagram of Haye's bridge, deduce the equation when the bridge is under balanced condition. (c) Explain Self-inductance can be measured using the Haye's bridge bridge. (d) In a four arms of Haye's A.C bridge, AB-Coil is unknown impedance, BC-Non reactive resistance of 1000Ω , CD- Non reactive resistance of 833Ω in series with a standard capacitor of $0.38 \mu f$, DA is a non-reactive resistance of $16,800 \Omega$. if the supply frequency is 50 Hz , determine the inductance and resistance at the balance condition.
2. (a) What is a multimeter? Name a type of Ohmmeter used for measuring (i) low resistance (ii) high resistance value. (b) Briefly explain the operation of attractive and repulsive type moving-iron indicating instrument with the aid of appropriate diagrams. (c) Derive the expression for torque equation in a moving iron instrument when there is a small increment in the current supplied to the instrument. Comment upon the nature of scale. (d) The moving system is provided with control springs. Find the deflection of a moving-iron Ammeter having the following data: Control Spring Constant is $8 \times 10^{-6} \text{ Nm/rad}$, Current is 6 A , $L = (6 + 3\theta - 0.5\theta^2) \mu\text{H}$.
3. (a) With a neat diagram, explain the construction and principle of operation of a dynamometer type wattmeter. (b) An electro-dynamometer wattmeter is employed to measure power in a single circuit, if the load voltage is 200 V and the load current is 5 A at a lagging power factor of 0.1 . The wattmeter potential coil has a resistance of $12,000 \Omega$ and inductance of 120 mH . Determine the percentage error in the wattmeter reading. (c) Give the possible circuit diagram of connecting pressure coil of wattmeter and compare the error. (d) Briefly describe how the measurement of Q-factor may be achieved. A Q-meter measures the Q-factor of a series L-R-C circuit to be 200 at a resonance frequency of 200 kHz . If the capacitance of the Q-meter is set to 300 pF determine (i) the inductance L ; (ii) the resistance R of the inductor.

SECTION B: Answer any two questions from this section

1. (a) Differentiate between Electrical and Electronic Instruments.
 (b) Give three advantages of Electronic Instruments over Electrical Instruments.
 (c) AC voltmeters can broadly be divided into three categories, name the categories.
 (d) What is an electronic recorder? Why is the strip chart recorder also called the X-t recorder?
2. (a) Draw the block diagram of the True RMS Reading Voltmeter. What is the function of the thermocouple in the diagram? What is the specific function of the balancing thermocouple?
 (b) How does the True RMS Reading Voltmeter measure the true value of non-sinusoidal waveform?
 (c) What are the factors to be considered in the selection of analog voltmeter?
 (d) What is noise in measurement?
3. (a) What are the common characteristics of the various types of signal generators?
 (b) Briefly describe how an oscillator produces an output signal without an external input. What are the conditions for sustained oscillation?
 (c) Differentiate between Alternator, Amplifier, and Oscillator.
 (d) The 555 timer can be configured as an astable or free-running multivibrator. Diagrammatically show how the 555 timer can be configured or connected as an astable multivibrator. In not more than 10 bullet points describe the operation of the 555 timer in the astable mode.

ECE 302 EXAM 2013/2014

FEDERAL UNIVERSITY OF TECHNOLOGY OWERRI
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
RAIN SEMESTER 2013/2014 EXAMINATION
ECE 302: ELECTRICAL MEASUREMENT AND MEASURING INSTRUMENT
INSTRUCTIONS: : ANSWER FOUR QUESTIONS ONLY Time: 2 Hrs.

OBT

1a. Mention and explain the three basic sections of a measuring instrument. (b) Explain the following terms used in characterizing an instrument system (i) Accuracy (ii) Resolution (iii) Hysteresis (iv) Sensitivity (v) Precision (c) Mention and explain two sources of random errors and five sources of systematic errors in an instrument, (d) A set of independent current measurements taken by four observers was recorded as 117.11A, 117.08A and 117.05A calculate (i) the average current (ii) the range of error (e) Measurement of a resistance over a period of time gave the following results in ohms 10.16, 10.15, 10.14, 10.05, 10.00, 9.99. What is (i) the arithmetic mean (ii) the mean deviation (iii) the standard deviation for the resistance over that period of time.

2a. Mention and explain the functions of the various parts of a permanent magnet moving coil meter (b) List the three torques produced in a moving coil instrument. What are the functions of this torques? (c) With simple diagrams show how the range of a basic PMMC meter can be extended as (i) An Ammeter (ii) A Voltmeter (d) A basic movement meter with internal resistance $R_m = 100\Omega$ and full scale deflection current $I_m = 1\text{mA}$ is to be converted into a multirange dc voltmeter with voltage ranges of 0 – 15v, 0 – 60v, 0 – 250v and 0 – 600v. Draw the circuit for such a multirange voltmeter with multipliers of R_1, R_2, R_3 and R_4 and determine the values of these resistances:

3 Explain with diagram the principles of operation of (i) electrostatic voltmeter (ii) electro dynamometer. State their basic advantages over the moving iron meters and PMMC.

4. What will be the out-of-balance current through the galvanometer for the wheatstone bridge shown in fig.4. If the galvo has a current sensitivity of 10mm/MA and an internal resistance of 100Ω , calculate the deflection of the galvo.

(b) Draw a circuit diagram of Maxwell-wien bridge. A Maxwell-wien bridge with a 1KHz ac supply is used to determine the inductance and series resistance of an inductor. At balance the bridge arms are AB $2.0\text{M}\Omega$ in parallel with $10\text{K}\Omega$, BC 200Ω , CD the inductor, and DA 300Ω . What are the inductance, series resistance and Q-factor of the inductor. (c) Explain how the following measurements can be carried out using basic counter. (i) Period measurement (ii) Time interval measurement (iii) Frequency measurement

5a. Explain using well drawn circuit/block diagrams the operation of (i) successive approximation type voltmeter (ii) digital frequency meter. (b) What is a signal generator. Mention two conditions for a circuit to function as an oscillator. (c) Draw a Colpitt LC oscillator and use it to explain how the conditions in 5(b) are satisfied. (d) Draw the block diagram of a basic electronic counter. Explain the function of each block.

6a. Draw a basic diagram of a Cathode Ray Oscilloscope. Explain using diagrams and equations the following functions in an Oscilloscope (i) focusing (ii) deflection (horizontal/vertical) (iii) beam acceleration (iv) Brightness control (b) Why is signal to be measured connected through the vertical deflecting plates.

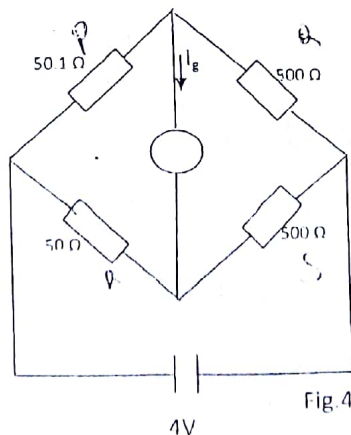


Fig.4

AW

500
10 x 10^-6 x 10^-3
 $V = I \cdot R$
 $Z = R$

085

ECE 302 EXAM 2012/2013

FEDERAL UNIVERSITY OF TECHNOLOGY, OWERRI
SCHOOL OF ENGINEERING AND ENGINEERING TECHNOLOGY
DEPARTMENT OF ELECTRICAL/ELECTRONIC ENGINEERING
SECOND SEMESTER EXAM, 2012/2013 SESSION
COURSE: ECE 302: INSTRUMENTATION AND MEASUREMENT

085

10

INSTRUCTION: ANSWER 4 QUESTIONS.

TIME: 2 HRS

- ✓ 1a. (i) Distinguish between these two types of Electrical and Electronic Measuring Instruments a). Ammeter b). Voltmeter. (ii) what are the similarity between a and b
- 1b. The impedance of an a.c bridge $Z_1 = 400\Omega \angle 50^\circ$, $Z_2 = 200\Omega \angle 40^\circ$, $Z_3 = 800\Omega \angle -50^\circ$, $Z_4 = 400\Omega \angle 20^\circ$, find whether the bridge is balance under these condition or not.
- ✓ 1c. List three conditions necessary for a balanced bridge circuit.
- ✓ 2. A bridge with a 1kHz a.c supply is used to determine the inductance and series resistance of an inductor. At balanced the bridge arms are MN $2.0\mu F$ in parallel with $10k\Omega$. NO 200Ω , OP the inductor, and PM 400Ω . (i) What are the inductance, resistance and Q-Factor of the inductor? (ii) What is the name of this bridge and give reason for chosen the name.
- ✓ 3a. Comment on the following: (i) What are the three essential elements of an instrument. (ii) Why are direct measuring instruments most widely used in engineering practice. (iii) What is the difference between analog and digital signals. (iv) List the classification of instruments based on their functions. (v) What is meant by transducer.
- 3b. A Multimeter having an input resistance of $25k\Omega$ is used to measure the voltage across a circuit having an output resistance of $1.0k\Omega$ and an open-circuit voltage of 12V. Find the error in measurement.
- 4a. Comment on the following: (i) What are the essentials of indicating instrument (ii) Why is control mechanism provided in an indicating instrument (iii) What are the various techniques by which damping torque is provided in electrical instrument (iv) What are the materials used for control springs (v) Why is damping mechanism provided in electrical measuring instruments?
- 4b. (i) Draw a circuit diagram for measurement of low impedance component using Q-meter. Explain the procedures involved in carrying out the test. (ii) Compare a Hartley Oscillator and a Colpitt oscillator using circuit diagram only
- ✓ 5a. (i) Mention 2 areas of application of the Cathode Ray oscilloscope (CRO) (ii) What are the 2 parts of the CRO, and briefly state the component parts and their functions.
- 5b. (i) Differentiate between the fluorescent characteristic of a material and its phosphorescence characteristic. (ii) What is the use of Delay-Line circuit?
- 6a. (i) The X-deflecting plates in a CRT are 30mm long and 5mm apart. The centre of the plates is 15cm from the screen. Determine the deflection sensitivity and deflection factor of the CRT if the accelerating voltage is 2000V. (ii) Draw deflection patterns for the following conditions (assume that vertical and horizontal voltage components V_v & V_h are sinusoidal, with equal amplitude and frequency)
- $V_v = 0^\circ$; $V_h = 180^\circ$
 $V_v = 90^\circ$; $V_h = 180^\circ$
 $V_v = 0^\circ$; $V_h = 0^\circ$
- 6b. The voltage across the horizontal deflection plates of the cathode ray oscilloscope is $V_1 \sin(\omega t + \Phi_1)$ and that across the vertical plates is $V_2 \sin(\omega t + \Phi_2)$. Prove that the trace on the screen is an ellipse.

ECE 302 EXAM 2011/2012

Due Electronics and Electrical Measurements / Instrumentation

TEXTBOOK: Electrical/Electronic measurements / Techy by W. Bolton

OBS

FEDERAL UNIVERSITY OF TECHNOLOGY OWERRI
ELECTRICAL/ELECTRONIC DEPARTMENT
ECE302 ELECTRICAL/ELECTRONIC INSTRUMENTATION PRINCIPLES
RAIN SEMESTER EXAMINATION 2011/2012

TIME ALLOWED: 2 HOURS

INSTRUCTION: ANSWER FOUR QUESTIONS ONLY.



Define the following terms as regards to electrical instrumentation: (i) Resolution (ii) Accuracy (iii) Hysteresis error

(iv) Precision (v) repeatability

It is desired to measure the value of current in 1000Ω resistor as shown in fig.Q1 by connecting an Ammeter of 200Ω resistance. Determine: (i) actual value of current (ii) measured value of current (iii) percentage error in the measurement (iv) accuracy.

Draw the circuit diagrams of the following DC Voltmeters: (i) Direct coupled amplifier transistorized dc voltmeter (ii) Wien bridge triode vacuum tube voltmeter (VTVM).

A meter movement has an internal resistance of 100Ω and requires $1mA$ dc for full scale deflection. Shunting resistance R_{sh} is connected across the movement has a value of 100Ω . Diodes D_1 and D_2 have an average forward resistance of 400Ω each and assumed to have infinite resistance in the reverse direction. For a $10V$ ac range evaluate (i) the multiplier value (ii) the voltmeter sensitivity on the ac range. Use fig.Q2

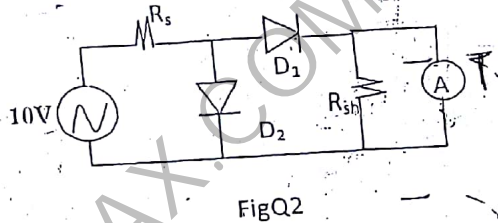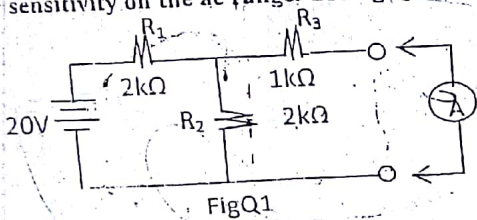

Q1. What is potentiometer?

A bridge with $4kHz$ a.c supply is used to determine the inductance and series resistance of an inductor. At balance bridge arms are MN $2.0\mu F$ in parallel with $10k\Omega$, NO 200Ω , OP the inductor, and PM 400Ω . What are the inductance and Q-factor of the inductor? What is the name of this bridge and give reason for chosen the name. maxwell Wien bridge

Q2. a. i. Mention any 2 applications of the Cathode Ray oscilloscope (CRO)

ii. Define the following: (1) AQUADAG (2) LISSAJOUS PATTERNS
iii. Differentiate between the fluorescent characteristic of a material and its phosphorescence characteristic.
iv. What is the use of Delay-Line circuit?

* Q3. (i) The X-deflecting plates in a CRT are $15mm$ long and $6mm$ apart. The centre of the plates is $20cm$ from the screen. The accelerating voltage is $2500V$. Determine the deflection sensitivity and deflection factor of the CRT.

* (ii) Draw deflection patterns for the following conditions (assume that vertical and horizontal voltage components V_v & V_h are sinusoidal, with equal amplitude and frequency)

$$V_v = 0^\circ; V_h = 180^\circ \quad V_v = 90^\circ; V_h = 180^\circ \quad V_v = 0^\circ; V_h = 0^\circ$$

c. The voltage across the horizontal deflection plates of the cathode ray oscilloscope is $V_1 \sin(\omega t + \Phi_1)$ and that across the vertical plates is $V_2 \sin(\omega t + \Phi_2)$. Prove that the trace on the screen is an ellipse.

Q4. With suitable block diagrams identify the major difference between Frequency and Period measurements.

$$LSD = \frac{2y}{V_v} \cdot \frac{V_h}{V_v}$$

State how Period measurement can be modified for Time Interval measurement.

Q5. Mention any transducer and its area of application.

Q6. In a typical Galvanometric Recorder, show how controlling and deflecting torques are related.

Q7. The above instrument has a coil of resistance 15Ω and a given current causes a 45° deflection. Assuming constants for the instrument and springs are 1000 and 20 respectively, determine the voltage the instrument will record when used as a voltmeter.

$$= \frac{LSD}{24d}$$