

FEDERAL UNIVERSITY OF TECHNOLOGY, OWERRI  
SCHOOL OF SCIENCE  
DEPARTMENT OF PHYSICS

2013/2014 HARMATTAN SEMESTER EXAMINATION  
PHY 201: APPLIED ELECTRICITY 1  
ANSWER ALL QUESTIONS


TIME: 3 HOURS

Surname	Reg. No.
Other names	Department


- Define potential difference between two points in a circuit.
- A battery pushed 240 coulombs through a circuit in 30s. calculate the current in the circuit
- Copper wires in houses typically have a diameter of about 2.5mm. How long a wire would have a  $2.0\Omega$  resistance? (Conductivity  $\sigma$  for Cu =  $5.95 \times 10^7 (\Omega m)^{-1}$ )
- What are the four colour bands of a resistor with resistance  $(82 \pm 8.2)k\Omega$ ?
- An electric heater draws a steady 12A on a 120V line. How much does it cost per 30 days if it operates 2.0h per day and the electric company charges N10.00k per kWh
- Two coils which are close together have a mutual inductance of 230mH. If the emf in coil 1 is 100V, what is the rate of change of the current in coil 2
- Calculate the potential difference across  $R_1$  in the circuit segment below



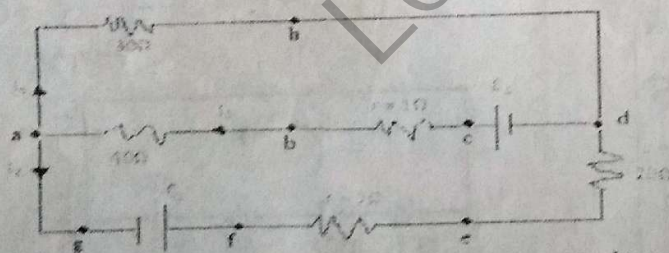
- In a circuit loop containing resistance  $R$ , if the resistance is traversed in the direction of the current  $I$ , the potential drop is
- Using loops  $ahdcba$  and  $ahdefga$  on the circuit below, determine the values of  $\mathcal{E}_1$  and  $\mathcal{E}_2$  if  $I_1$ ,  $I_2$  and  $I_3$  are  $-0.8626A$ ,  $2.5960A$  and  $1.7278A$  respectively



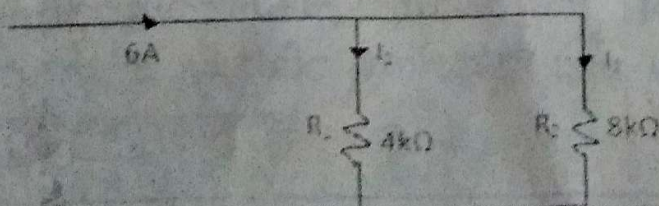- Two resistors  $4\Omega$  and  $5\Omega$  in series are connected to a battery of emf 4V and internal resistance  $1.0\Omega$ . Find the current in the circuit
- Three resistors  $R_1=100\Omega$ ,  $R_2=40\Omega$  and  $R_3=60\Omega$  are connected in series across a voltage source of 20V. What is the voltage drop across  $R_3$
- Calculate  $I_2$  from the figure below



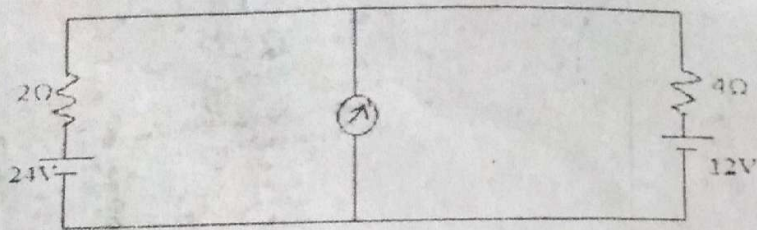
(13) Using the superposition theorem, find the current through the  $2\Omega$  resistor in the circuit below \_\_\_\_\_




(14) When maximum power transfer is achieved, efficiency is \_\_\_\_\_

(15) In Thevenin's theorem, a dc network can be replaced by an equivalent circuit consisting of \_\_\_\_\_

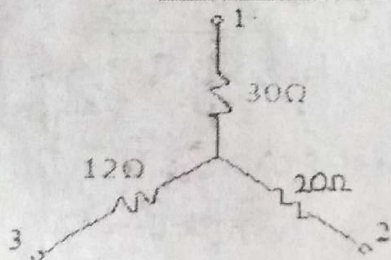(16) The three resistances  $30\Omega$ ,  $20\Omega$  and  $12\Omega$  are star-connected as shown below. Convert the star connection to delta connection \_\_\_\_\_



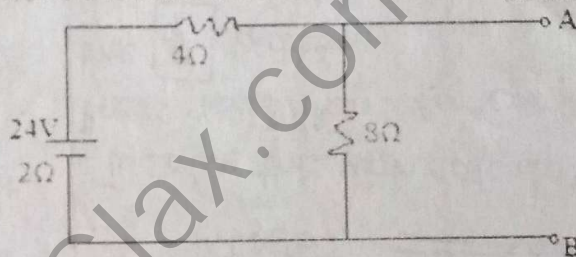(17) Deduce the Norton's equivalent between terminals A and B from the circuit below \_\_\_\_\_



(18) A resistive load,  $R_L$  draws the maximum power from a 24V,  $4\Omega$  voltage source. The value of this maximum power is \_\_\_\_\_

(19) Define the root mean square (rms) value of an alternating quantity \_\_\_\_\_

(20) The average value of an alternating voltage is 20V. Calculate the root mean square (rms) value of the voltage \_\_\_\_\_

(21) If the equation of an alternating voltage is given by  $e = 50\sin 2\omega t$ , what is the frequency \_\_\_\_\_

(22) What is the equation of a 50Hz current sine wave having an rms value of 60A \_\_\_\_\_

(23) State the difference between a leading and a lagging alternating quantity \_\_\_\_\_

(24) An alternating current is given by the expression  $i(t) = 30\sin(157t + \pi/3)$ , calculate the period \_\_\_\_\_

(25) An ac voltage of 50Hz frequency has a peak value of 100V. Find the average value of the voltage \_\_\_\_\_

(26) A  $30\mu\text{F}$  capacitor is connected across a 400V, 50Hz supply, calculate the reactance of the capacitor \_\_\_\_\_

(27) State the condition for series resonance \_\_\_\_\_

(28) An RLC circuit consists of a resistance of  $100\Omega$ , an inductance of 1000mH and a capacitance of  $100\mu\text{F}$ . If a voltage of 100V is applied across the combination, find the resonance frequency \_\_\_\_\_

(29) A resistance of  $50\Omega$ , an inductance of 0.15H and a capacitance of  $100\mu\text{F}$  are connected in parallel across a 100V, 50Hz supply. Calculate the current in each branch \_\_\_\_\_

(30) A current  $I = 1.8\cos 377t$  flows in a series LR circuit in which  $L = 3.85\text{mH}$  and  $R = 1.35\text{k}\Omega$ . What is the average power dissipation \_\_\_\_\_

(31) When is the complex expression for impedance Z capacitive \_\_\_\_\_

(32) In a given R-L circuit,  $R = 35\Omega$  and  $L = 1\text{H}$ . Find the current flowing through the series circuit at 50Hz when the voltage  $V = 110 \angle 30^\circ$  volts is applied across the circuit \_\_\_\_\_

(33) An alternating voltage  $(8 + j6)\text{V}$  is applied to a series ac circuit and the current flowing is  $(2 + j5)\text{A}$ . Find the impedance \_\_\_\_\_

(34) If an alternating current is given as  $37.74 \angle -32^\circ$ , calculate the power factor \_\_\_\_\_

(35) Two impedances given by  $Z_1 = (10 + j5)$  and  $Z_2 = (8 + j6)$  are joined in parallel and across a voltage of  $V = (200 + j0)$  volts. Calculate the phase of the total current \_\_\_\_\_

## 2013/2014 EXAM SOLUTIONS

1) The potential difference between two points in a circuit is the difference in potential energy per unit charge between the two points.

2 Given  $Q = 240\text{C}$ ,  $t = 30\text{s}$

$$I = \frac{Q}{t} = \frac{240}{30} = \underline{8\text{A}}$$

3  $\rho = \frac{RA}{L}$ ;  $L = \frac{RA}{\rho}$

$R = 2\Omega$ ,  $d = 2.5\text{mm} = 0.0025\text{m}$ ,  $\rho = \frac{1}{\sigma} = \frac{1}{5.94 \times 10^7}$

$$\therefore A = \frac{\pi d^2}{4} = \frac{\pi (0.0025)^2}{4} = 4.91 \times 10^{-6} \text{m}^2$$

$$\therefore L = \frac{2 \times 4.91 \times 10^{-6}}{(5.94 \times 10^7)^{-1}} = \underline{\underline{584.14\text{m}}}$$

4  $(82 \pm 8.2)\text{k}\Omega = (82 \pm 8.2) \times 10^3 \Omega$

1st digit - 8 = Grey

2nd digit - 2 = Red

Multiplier -  $\times 10^3$  = Orange

\* Notice that 8.2 is 10% of 82, Therefore tolerance of 10% = Silver

Thus the four colours are Grey, Red, Orange, Silver

5  $I = 12\text{A}$ ,  $V = 120\text{V}$ ;

$$P = IV = 12 \times 120 = 1440\text{W}$$

Since the heater operates at 2hrs Per day for 30 days, therefore it operates for a total of

$$2 \text{rs} \times 30 \text{days} = 60\text{hrs}$$

Thus the total cost is

$$1.44\text{kW} \times 60\text{hr} \times 10/\text{kWh} = \underline{\underline{864}}$$

6  $V = L \frac{di}{dt}$ ;  $\frac{di}{dt} = \frac{V}{L}$

but  $V = 100\text{V}$ ,  $L = 230\text{mH} = 230 \times 10^{-3}\text{H}$

$$\frac{di}{dt} = \frac{100}{230 \times 10^{-3}} = \underline{\underline{434.78\text{A/s}}}$$

7) From KCL,  $I_4 = I_1 + I_2 + I_3$

but  $I_1 = I_4 - (I_2 + I_3)$

$$= 11 - (2 + 4) = 5\text{A}$$

$$V_1 = I_1 R_1 = 5 \times 10\text{k}\Omega = \underline{\underline{50\text{kV}}}$$

8)  $-IR$

9) From loop ahdcba,

$$-30I_1 + \mathcal{E}_2 - I_3 - 40I_3 = 0$$

$$\mathcal{E}_2 = 30I_1 + 41I_3$$

$$\mathcal{E}_2 = 30(-0.8626) + 41(1.7278) = \underline{\underline{44.9618\text{V}}}$$

from loop ahdefga,

$$-30I_1 + 20I_2 + I_2 - \mathcal{E}_1 = 0$$

$$\mathcal{E}_1 = -30I_1 + 21I_2$$

$$\mathcal{E}_1 = -30(-0.8626) + 21(2.5960) = \underline{\underline{80.4\text{V}}}$$


10)  $E = (R+r)I$

$$I = \frac{E}{R+r} = \frac{4}{(4+5)+1} = \frac{4}{10} = \underline{\underline{0.4\text{A}}}$$


11)  $V_3 = \frac{VR_3}{V_1+V_2+V_3} = \frac{20 \times 60}{100+40+60} = \underline{\underline{\frac{6\text{V}}{VDR}}}$

12)  $I_2 = \frac{IR_1}{R_1+R_2} = \frac{6 \times 4}{4+8} = \underline{\underline{2\text{A}}}$  (CDR)

13)

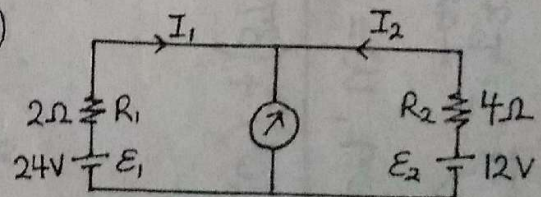


When  $E_1$  is acting alone

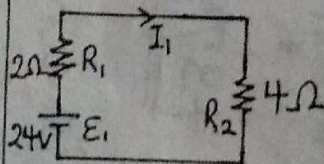

$$I_1 = \frac{E_1}{R_1+R_2} = \frac{24}{2+4}$$

$$I_1 = 4\text{A}$$

When  $E_2$  is acting alone,

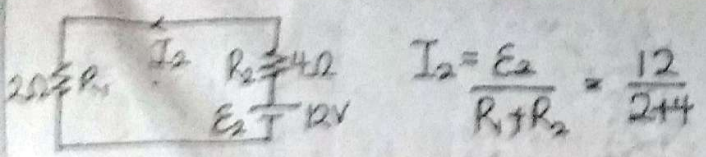

$$I_2 = \frac{E_2}{R_1 + R_2} = \frac{12}{2+4}$$


$$I_2 = 2A$$

Superposing the current through  $R_1$  is

$$I_1 - I_2 = 4 - 2 = \underline{2A}$$

$$\eta = \frac{\text{load power}}{\text{total power}} = \frac{P_L}{P_T}$$

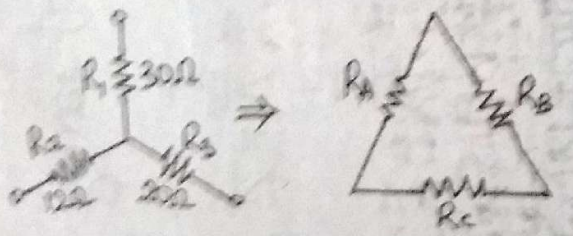... a voltage source  $V_{TH}$  in series with a resistor  $R_{TH}$ .




$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3} = \frac{(30)(12) + (30)(20) + (20)(30)}{20}$$

$$R_A = \underline{60\Omega}$$

$$R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2} = \frac{1200}{12} = \underline{100\Omega}$$

$$R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1} = \frac{1200}{30} = \underline{40\Omega}$$


Thus the delta connection is shown

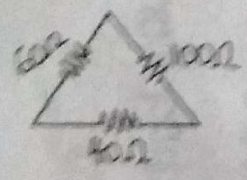

$$17) \frac{E}{R_1} = \frac{24}{4+2} = \frac{24}{6} = 4A$$

$$(4+2) \parallel 8 = \frac{6 \times 8}{6+8} = \frac{48}{14} = \underline{3.43\Omega}$$

Thus the Norton's equivalent circuit is

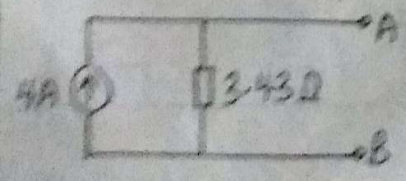

$$18) P_{L,max} = \frac{E^2}{4R_L} = \frac{24^2}{4 \times 4} = \underline{36W}$$

$$19) I_{rms} = \frac{I_m}{\sqrt{2}} \text{ and } V_{rms} = \frac{V_m}{\sqrt{2}} \text{ where}$$

$I_m$  and  $V_m$  are maximum currents and voltage respectively.

$$20) V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{20}{\sqrt{2}} = \underline{14.14V}$$

$$21) \omega = 2\pi f$$

$$f = \frac{\omega}{2\pi}$$

$$22) I_{rms} = \frac{I_m}{\sqrt{2}}, \text{ Given } I_{rms} = 60A$$

$$I_m = \sqrt{2} I_{rms} = 60\sqrt{2} = 84.85A$$

$$\omega = 2\pi f = 2\pi \times 50 = 100\pi$$

The equation of a current sine wave

$$I = I_m \sin \omega t$$

$$\therefore I_m = \underline{84.85 \sin 100\pi t}$$

23) The leading alternative quantity reaches the maximum value before the lagging alternating quantity.

$$24) T = \frac{2\pi}{\omega} = \frac{2\pi}{157} = \underline{0.04s}$$

$$25) E_{av} = 0.637 E_m = 0.637 \times 100 = \underline{63.7V}$$


$$26) X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 30 \times 10^{-6} \times 50}$$

$$X_C = \underline{106.1\Omega}$$

27) For series resonance,  $X_C = X_L$

$$28) f_0 = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{1000 \times 10^{-3} \times 100 \times 10^{-6}}}$$

$$f_0 = \underline{15.92Hz}$$

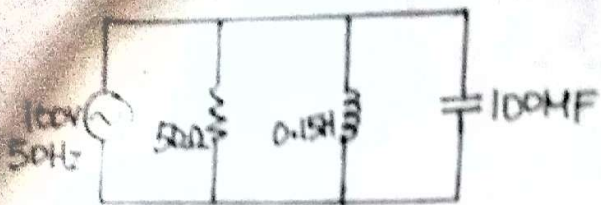

All the branches have the same voltage because they are in parallel

$$\text{Current across resistor } I_R = \frac{V}{R} = \frac{100}{50} = 2A$$

$$\text{Current across inductor } I_L = \frac{V}{X_L} = \frac{V}{2\pi fL}$$

$$I_L = \frac{100}{2\pi \times 50 \times 0.15} = 2.12A$$

$$\text{Current across capacitor } I_C = \frac{V}{X_C} = \frac{V}{\frac{1}{2\pi fC}}$$

$$I_C = \frac{100}{\left(\frac{1}{2\pi \times 50 \times 100 \times 10^{-6}}\right)} = 3.142$$

$$I_C = 3.142A$$

$$P_{av} = I_{av}V = I_{av}^2 Z = I_{av}^2 \sqrt{R^2 + X_L^2}$$

$$P_{av} = I_{av}^2 \sqrt{R^2 + (2\pi fL)^2} = I_{av}^2 \sqrt{R^2 + (\omega L)^2}$$

From the question,  $\omega = 377$ ,  $I_{av} = 1.8$

$$\therefore P_{av} = 1.8^2 \sqrt{(1.35 \times 10^3)^2 + (377 \times 3.85 \times 10^{-3})^2}$$


$$P_{av} = 4374W$$

This is when  $R = jX_L = 0$

because  $Z = R + j(X_L - X_C)$

Substituting  $R = jX_L = 0$

$Z = -jX_C$  which is purely capacitive

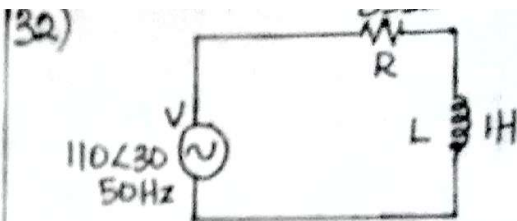

$$\text{Recall } e = E_m \sin(\omega t + \phi) = \frac{E_m}{\sqrt{2}} \angle \phi$$

$$\therefore 110 \angle 30^\circ = (\sqrt{2}) 110 \sin(2\pi f t + 30)$$

$$110 \angle 30^\circ = 155.6 \sin(100\pi t + 30)$$

$$V = IZ; I = \frac{V}{Z}$$

$$Z = \sqrt{R^2 + (2\pi fL)^2} = \sqrt{35^2 + (2\pi \times 50 \times 1)^2}$$

$$Z = 316.1 \Omega$$

$$\therefore I = \frac{V_m}{Z} = \frac{155.6}{316.1} = 0.49A$$

$$33) Z = \frac{V}{I} = \frac{8 + j6}{2 + j5} = 1.58 - j0.96$$

$$34) \text{ Power factor} = \cos \phi = \cos(-32^\circ)$$

$$\therefore \text{ Power factor} = 0.85$$

$$35) Z_1 || Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(10 + j5)(8 + j6)}{10 + j5 + 8 + j6}$$

$$Z_{12} = Z_1 || Z_2 = 4.5 + j2.81$$

$$I = \frac{V}{Z_{12}} = \frac{200}{4.5 + j2.81} = (32 - j20)A$$

Converting I to polar form,

$$(32 - j20)A = 37.7 \angle -32^\circ$$

Thus the phase  $\phi = -32^\circ$